

Design Of a Single-Stage Differential Amplifier

Name: Avinash Kumar


Roll No.:231040030

GIVEN SPECIFICATIONS:

VDD=1.8V, CL=10pF, Loop Gain= 35dB,
–3dB Bandwidth of V_O/V_i (min), CMRR(@DC)=80dB

CALCULATING G_m THEORETICALLY

① Calculating g_m

 


Given, open loop gain = 35dB
(L_A)

$$20 \log L_A = 35$$

$$L_A = 56.234$$

 ↳ Calculating loop gain by breaking the load from that, we will calculate g_m .



$$V_{test} = -g_m V_{test} (50k\Omega)$$

$$1 + (50k\Omega + 50k\Omega) g_m$$

$$L_A = \frac{-V_{test}}{V_{test}} = \frac{g_m (50k\Omega)}{1 + 2 g_m (50k\Omega)}$$

Given $W_{u, loop} = 2\pi \times 100 \times 10^6 \text{ rad/s}$


At $W_{u, loop}$, $L_A \rightarrow -1$

$$\Rightarrow 1 = \frac{g_m}{2 \times 2\pi \times 100 \times 10^6 \times 10^{-12}}$$


$$\Rightarrow g_m = 12.566 \text{ mS}$$

OPEN LOOP GAIN AND PHASE

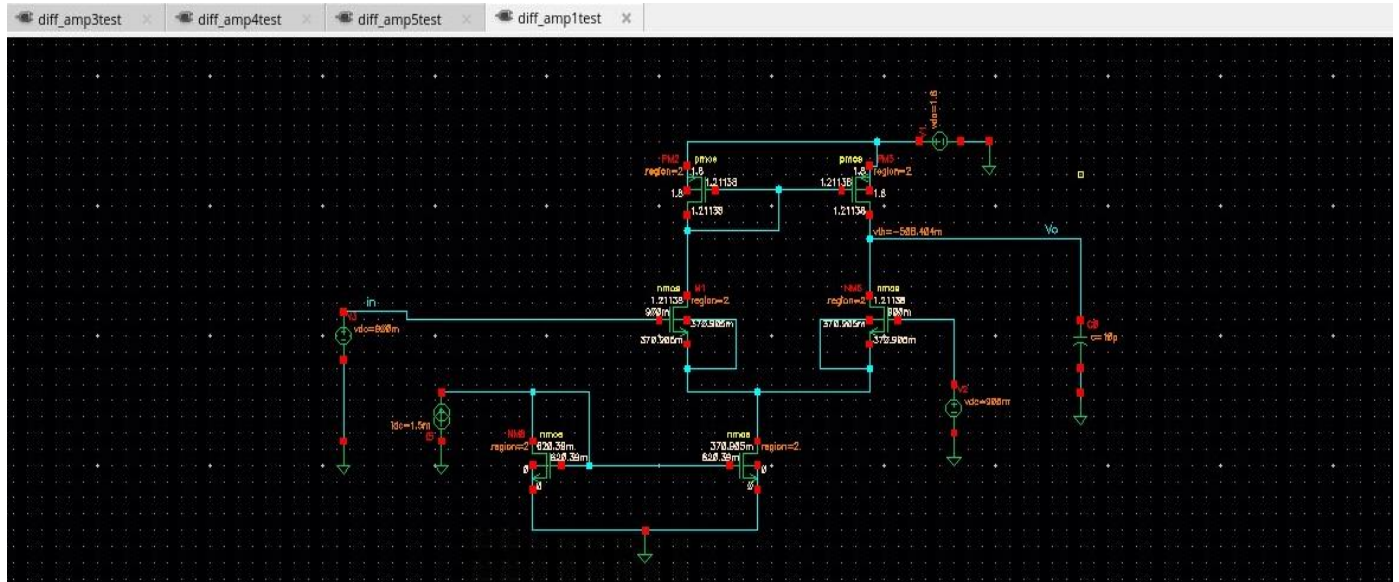
OPEN LOOP DC SCHEMATIC SHOWING REGION OF OPERATION OF EACH TRANSISTOR




OPEN LOOP AC SCHEMATIC

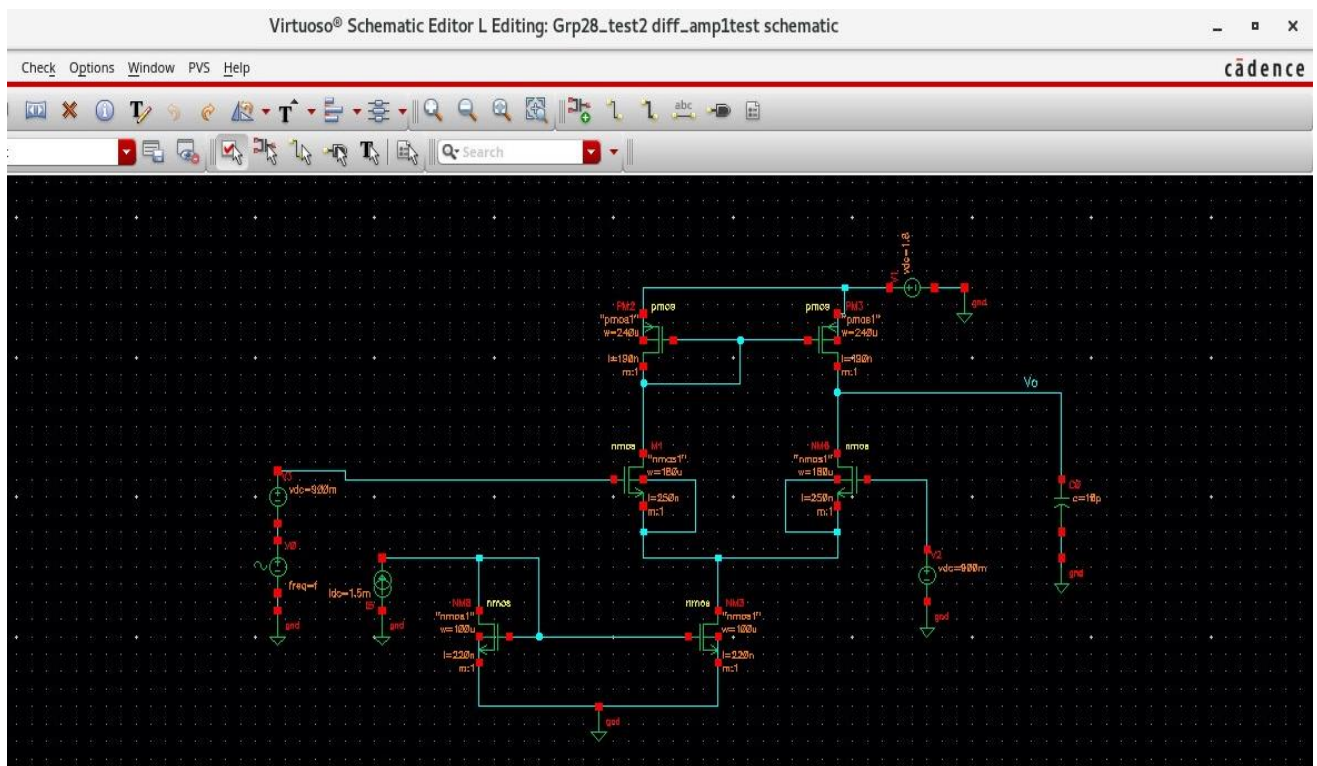

OPEN LOOP GAIN PLOT

 


OPEN LOOP PHASE PLOT

 


CLOSED LOOP GAIN AND PHASE

CLOSED LOOP SCHEMATIC

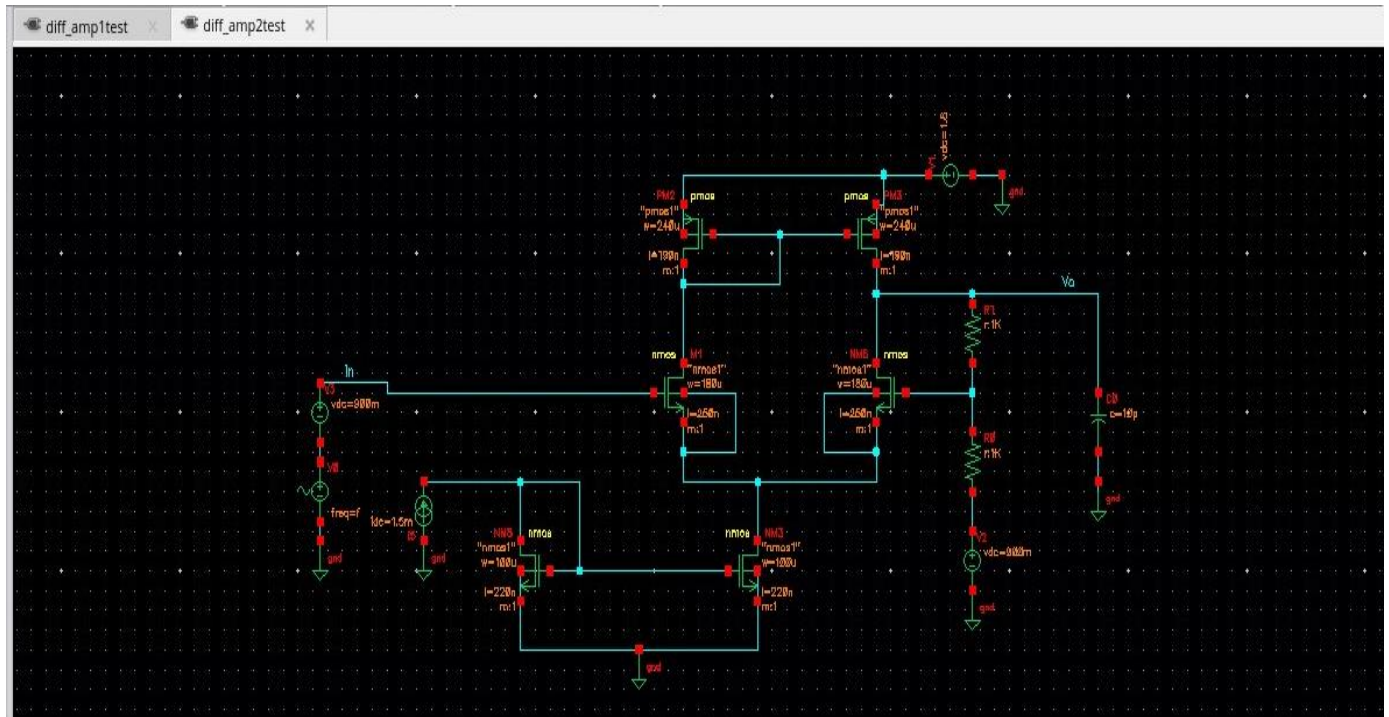

CLOSED LOOP GAIN AND PHASE PLOT

 


THEORETICALLY CALCULATED STEADY STATE ERROR

→ Calculation of steady state error


$$e_{ss} = \frac{1}{L(h)+1} \Rightarrow \frac{1}{56.234+1}$$

$$e_{ss} = 17.47 \text{ mV}$$

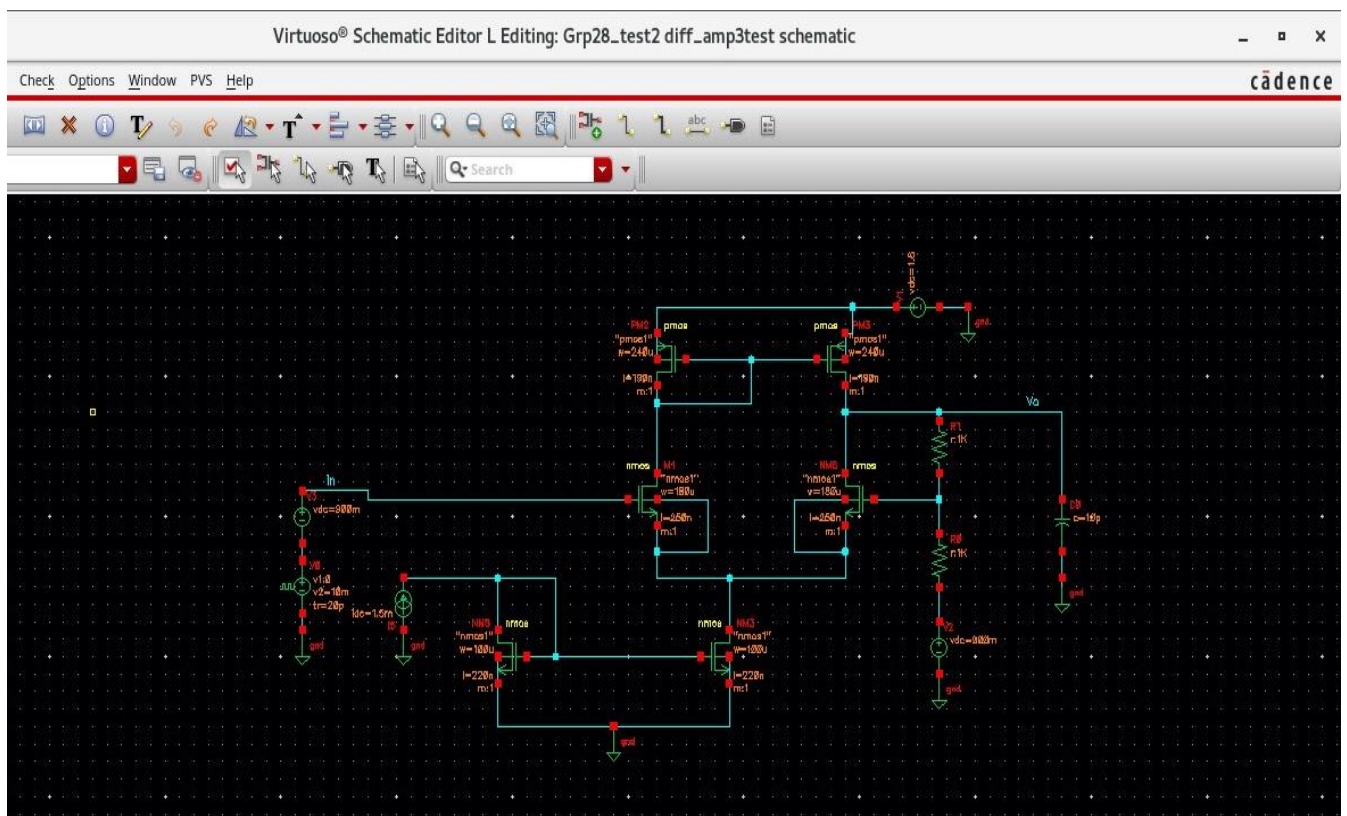SCHEMATIC FOR CALCULATION OF STEADY STATE ERROR




PLOT FOR TRANSIENT RESPONSE

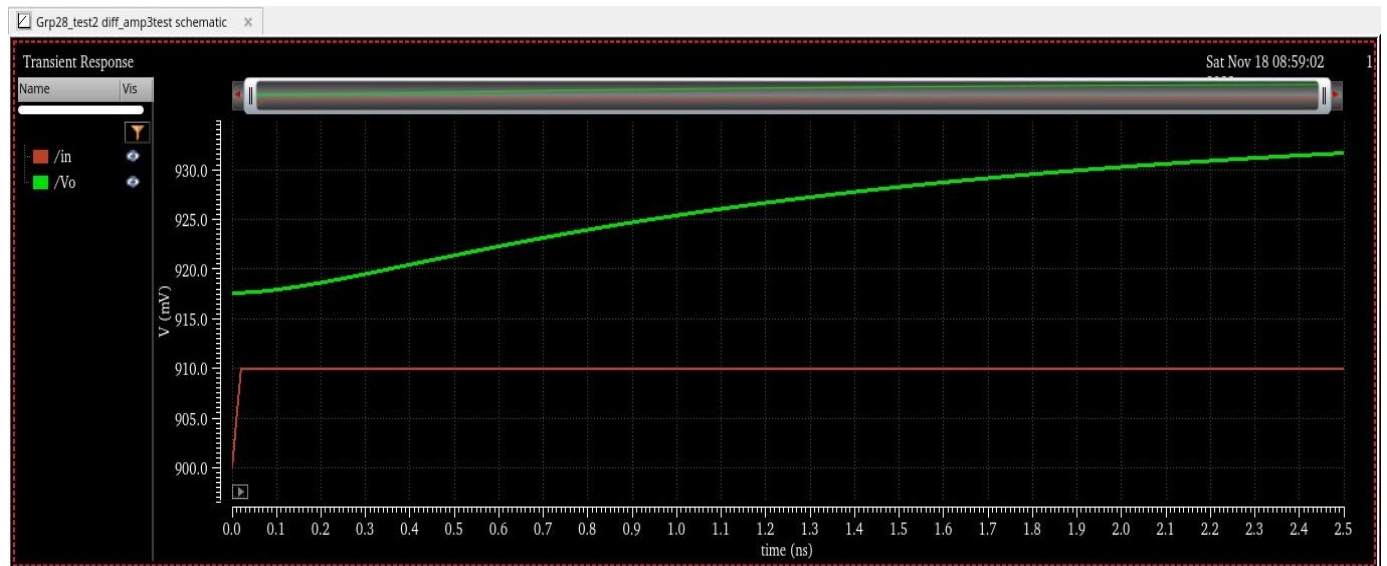


TRANSIENT RESPONSE OF THE NON-INVERTING AMPLIFIER WHEN $V_i = 150 \text{ mV} \cos(\Omega 3\text{dB } T)$

SCHEMATIC FOR TRANSIENT RESPONSE

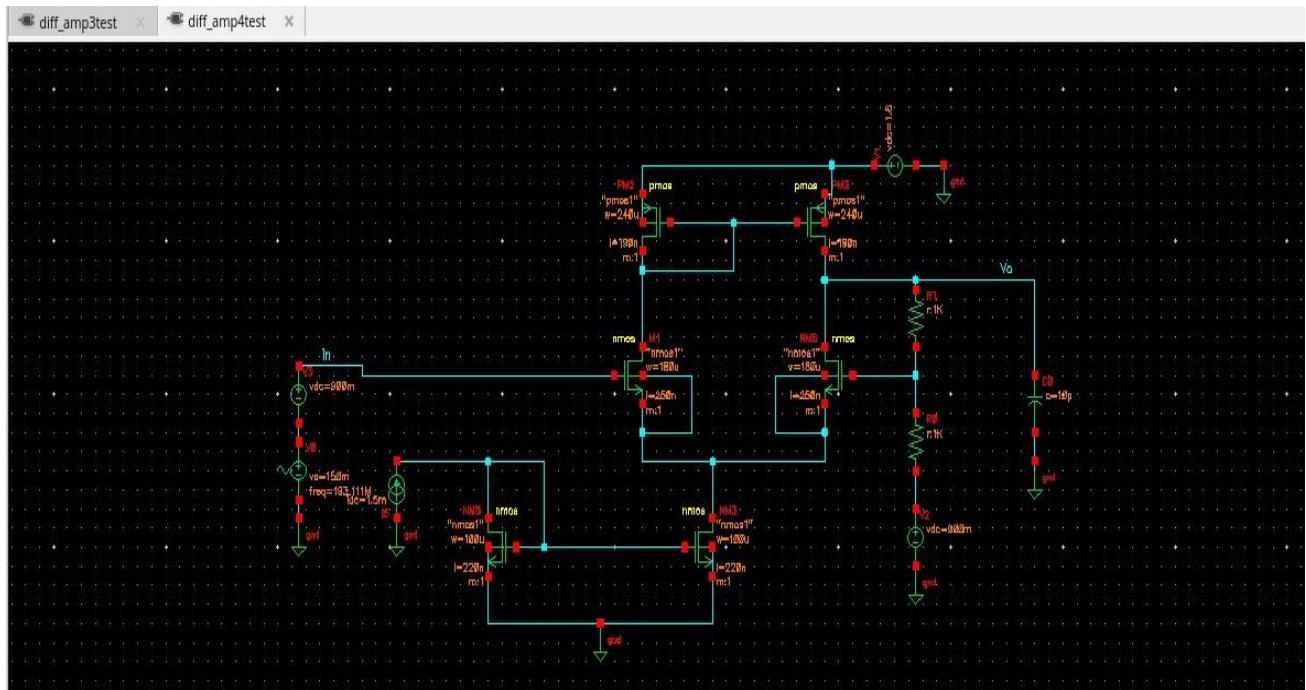


PLOT OF TRANSIENT RESPONSE

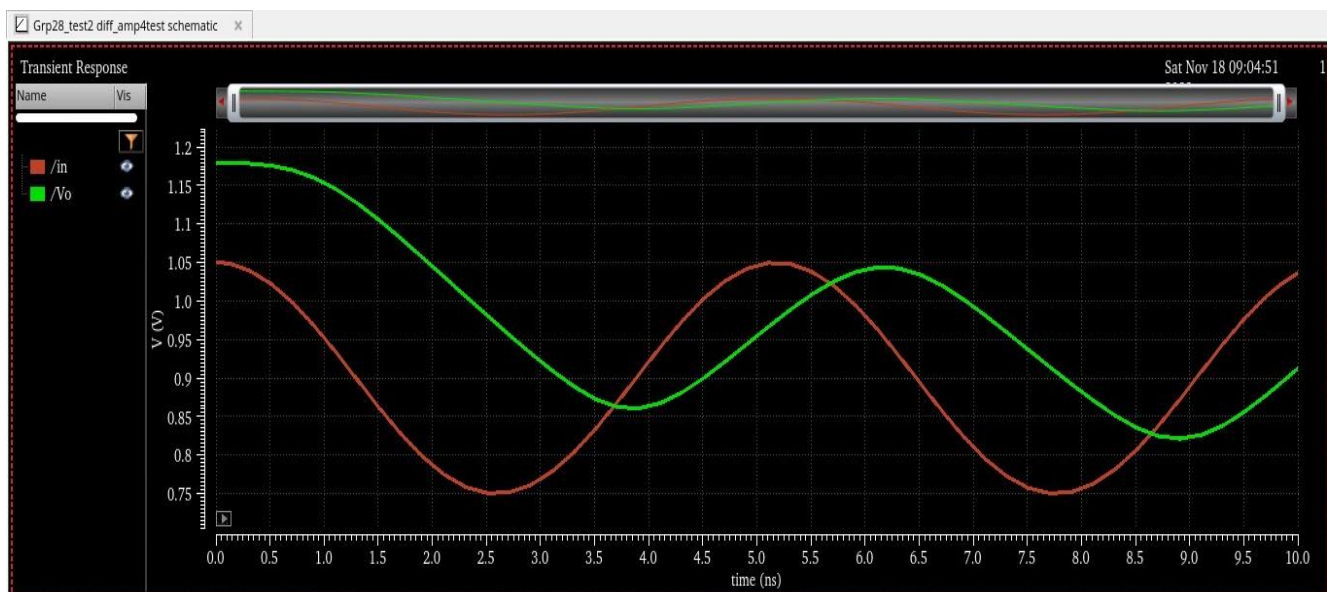


TRANSIENT RESPONSE OF THE NON-INVERTING AMPLIFIER WHEN $V_i = 150 \text{ mV} \cos((\Omega_{3\text{dB}}/10) \text{ T})$

SCHEMATIC FOR TRANSIENT RESPONSE

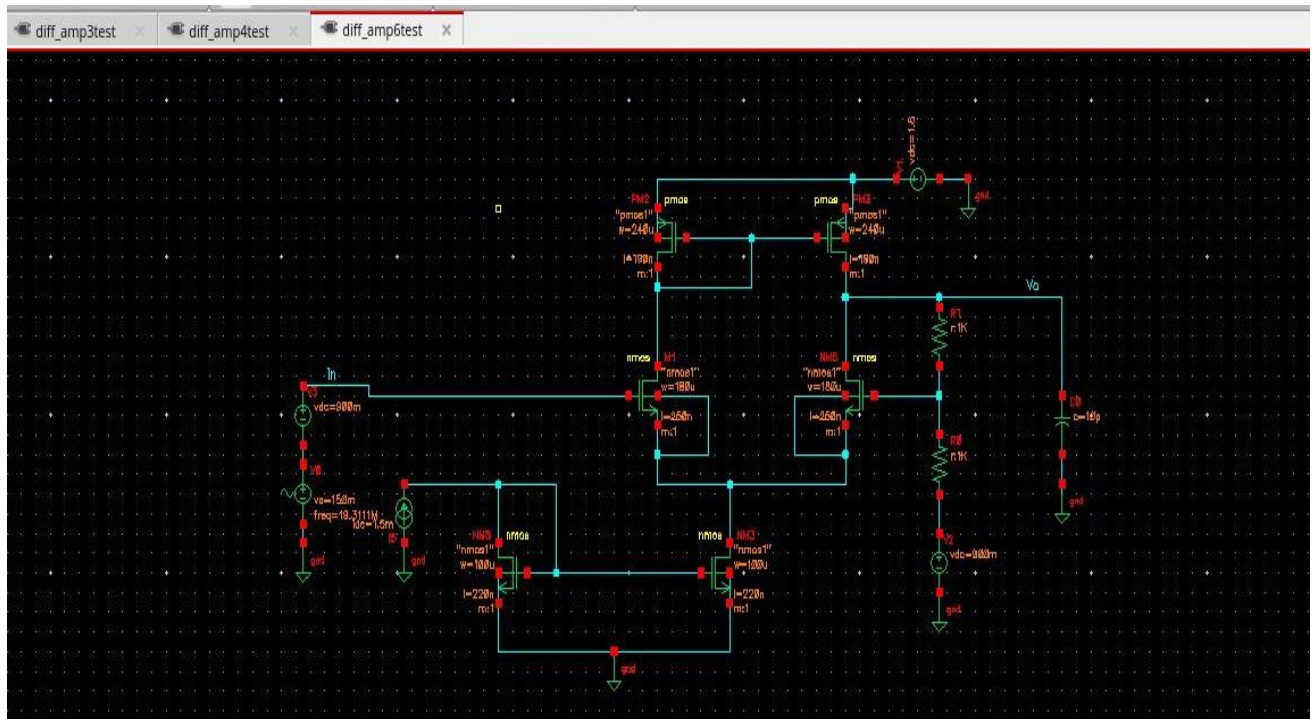


PLOT OF TRANSIENT RESPONSE

 


DIFFERENCE BETWEEN THE INPUT VOLTAGES OF THE DIFFAMP IN FIG. 1(A) FOR INPUTS 150 mV COS(ω_{3dB} T) AND 150 mV COS(($\omega_{3dB}/10$)T).


SCHEMATIC

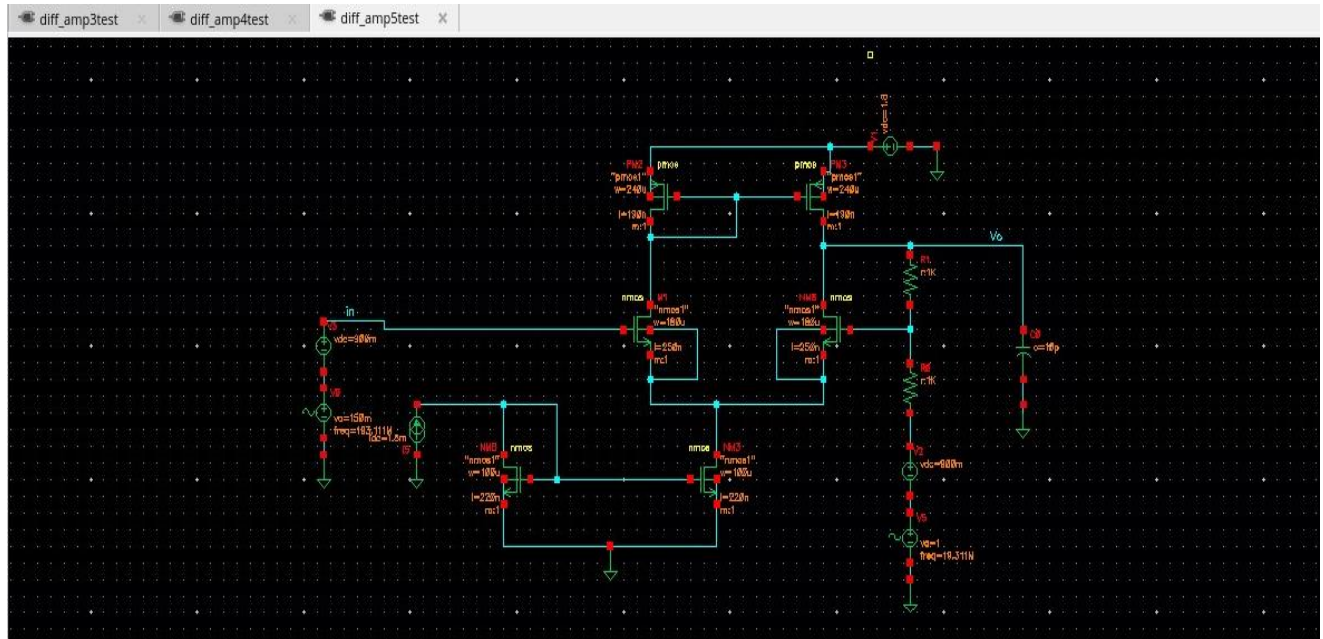

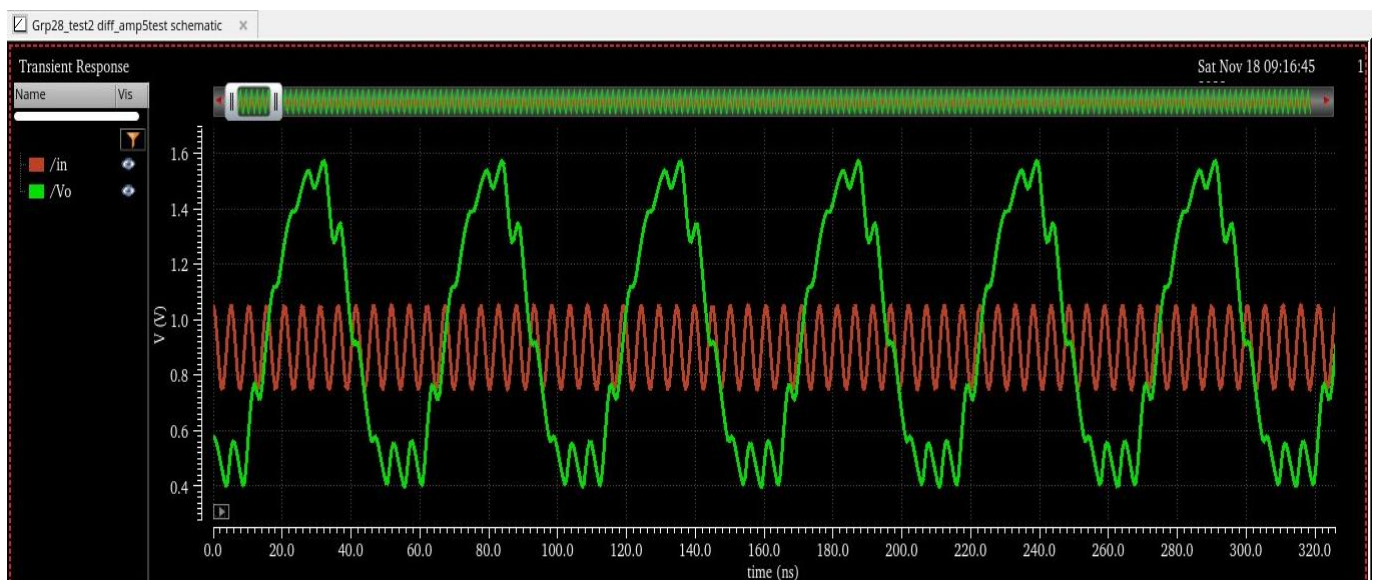PLOT OF THE DIFFERENCE BETWEEN THE INPUT VOLTAGES OF THE DIFFERENTIAL AMPLIFIER




TABULATION OF Gm, Gds, Cgs, Cgd, Vov

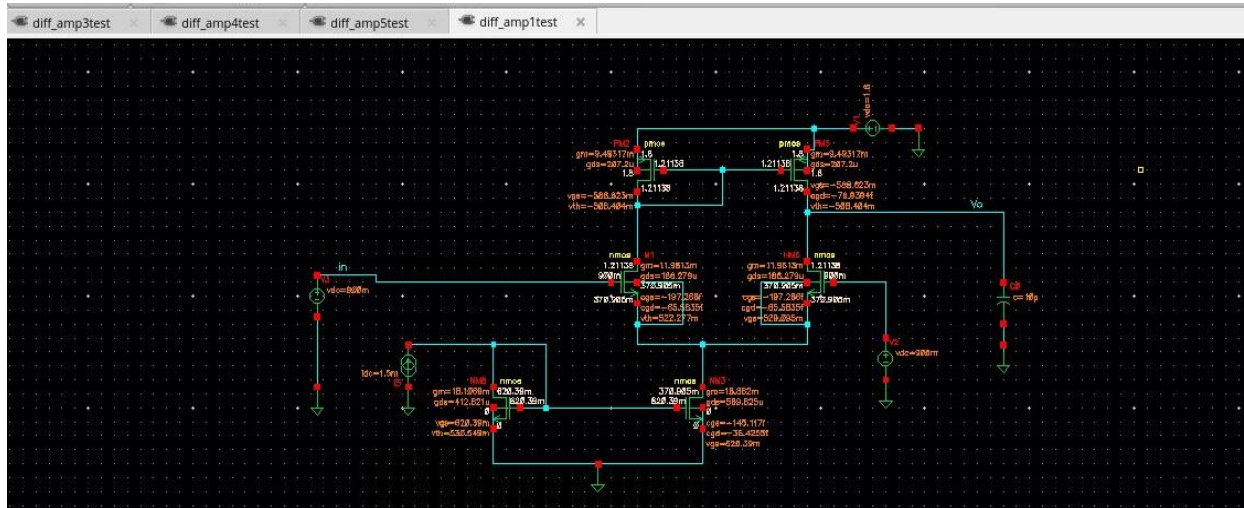

	gm	gds	Cgs	Cgd	Vov
M1(nmos)	11.963mS	186.279uS	197.26f F	65.58f F	6.818mV
NM6(nmos)	11.963mS	186.279uS	197.26f F	65.58f F	6.818mV
PM2(pmos)	9.49317mS	207.2uS	329.603f F	76.93f F	-80.219mV
PM3(pmos)	9.49317mS	207.2uS	329.603f F	76.93f F	-80.219mV
NM8(nmos)	18.1069mS	412.821uS	144.894f F	36.354f F	89.282mV
NM3(nmos)	11.693mS	569.825uS	!45.114f F	36.354f F	89.282mV

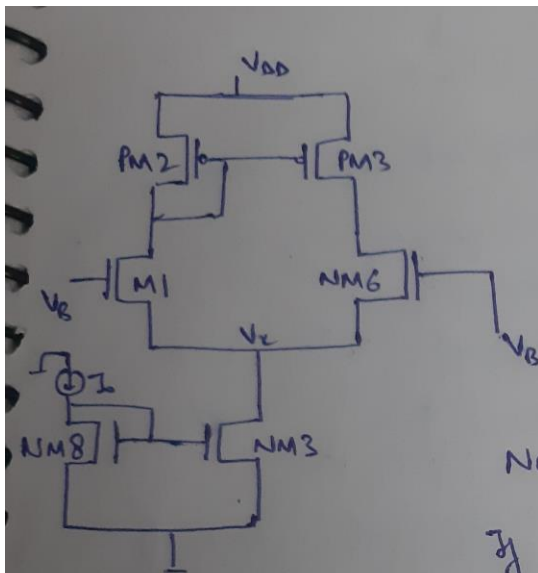THEOROTICAL CALCULATION OF ICMR+ AND ICMR-



$$\begin{aligned}
 V_{th} &= V_{DD} - |V_{th}|_{PM2} \\
 &= 1.8 - 0.5084 \\
 &\Rightarrow 1.2916 \text{ V}
 \end{aligned}$$

Now, M1 transistor will be saturated,

$$(V_B - V_{SB}) - V_{th}|_{M1} \leq V_m - V_{SB}$$

$$\Rightarrow V_B - 0.5222 \leq 1.2916$$

$$V_B \leq 1.8138$$

$$\Rightarrow \boxed{V_B \leq 1.8138 \text{ V}}$$

$$\boxed{ICMR^+ = 1.8138 \text{ V}}$$

and $\boxed{ICMR^- = V_{th}|_{M1} = 0.522 \text{ V}}$